



(SCHOOL NAME HERE)

NAME \_\_\_\_\_

AUTOMOTIVE TECHNOLOGY

**TITLE: Horn System Circuit**

TASK TYPE	NATEF TASK NUMBER	ACTION
Primary	NATEF Automotive Repair Task A6-G-1	Diagnose incorrect horn operation; perform necessary action.
Secondary	NATEF Automotive Repair Task A6-A-2	Identify and interpret electrical/electronic system concern; determine necessary action.
Secondary	NATEF Automotive Repair Task A6-A-7	Demonstrate the proper use of a digital multimeter (DMM) during diagnosis of electrical circuit problems, including: source voltage, voltage drop, current flow, and resistance.
Secondary	NATEF Automotive Repair Task A6-A-10	Check electrical circuits using fused jumper wires; determine necessary action.
Secondary	NATEF Automotive Repair Task A6-A-11	Locate shorts, grounds, opens, and resistance problems in electrical/electronic circuits; determine necessary action.
Secondary	NATEF Automotive Repair Task A6-A-13	Inspect and test fusible links, circuit breakers, and fuses; determine necessary action.
Secondary	NATEF Automotive Repair Task A6-A-14	Inspect and test switches, connectors, relays, solenoid solid state devices, and wires of electrical/electronic circuits; perform necessary action.

**PURPOSE:** To develop through repetition, a mastery of diagnosing electrical faults in a typical horn circuit.

**ACTIVITY:** Using the Automotive Electrical Diagnostic Trainer supplied by United Concept Trainers, have your instructor install a "fault(s) in the horn circuit. Determine fault(s) location with instructor approved electrical diagnostic tools. Record your diagnosis and conclusions below:

<u>1<sup>st</sup> fault activity</u> Circuit symptom _____ fault location _____ diagnosis _____
<u>2<sup>nd</sup> fault activity</u> Circuit symptom _____ fault location _____ diagnosis _____
<u>3<sup>rd</sup> fault activity</u> Circuit symptom _____ fault location _____ diagnosis _____
<u>4<sup>th</sup> fault activity</u> Circuit symptom _____ fault location _____ diagnosis _____
<u>5<sup>th</sup> fault activity</u> Circuit symptom _____ fault location _____ diagnosis _____
<u>6<sup>th</sup> fault activity</u> Circuit symptom _____ fault location _____ diagnosis _____

**Results:** Based on the above activity, what can you determine from diagnosing faulty electric cooling fan circuits?

\_\_\_\_\_

\_\_\_\_\_

